

# TUTORIAL 1 COMBINATIONAL LOGIC CIRCUIT

# Overview

---

- **We will review the following concept in this tutorial:**
- **Combinational logic circuit**
  - No memory, output(s) solely determined by input(s)
- **Truth table and logic function**
- **Two-level logic and PLA**
- **Simplification with Boolean Algebra and K-map**
- **Circuit design**
  
- **Work with two practical examples**
  - Bit comparator
  - Encoder

# Digital Logic Circuit

---

## ■ Two types of digital logic circuits inside a computer:

### □ **Combinational logic circuits**

- Logic circuits that do not have memory
- The output depends only on the current inputs and the circuit
- They can be specified fully with a truth table or a logic equation

### □ **Sequential logic circuits**

- Logic circuits that have memory
- The output depends on both the current inputs and the value stored in memory (called **state**)

# Circuit Design Process

---

- **A simple logic design process involves**
  - Problem specification
  - Truth table derivation
  - Derivation of logical expression
  - Simplification of logical expression
  - Implementation

# Review of Boolean Algebra

---


- **Boolean algebra consists of**
  - Boolean variables (with values equal to either '0' or '1' )
  - Binary operators: AND ( $\cdot$ ), OR ( $+$ ), NOT ( $'$ )
- **Any logic function can be expressed as a two-level logic expression, either as**
  - Sum-of-Products (SoP) representation, or
  - Product-of-Sums (PoS) representation
- **The AND, OR, and NOT operations form a functionally complete set (namely, **universal gates**), as they can specify any logic function.**

# Basic Laws of Boolean Algebra

Name	AND Form	OR Form
Identity Law	$1A = A$	$0 + A = A$
Null Law	$0A = 0$	$1 + A = 1$
Idempotent Law	$AA = A$	$A + A = A$
Inverse Law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative Law	$AB = BA$	$A + B = B + A$
Associative Law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive Law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption Law	$A(A + B) = A$	$A + AB = A$
De Morgan's Law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}\bar{B}$

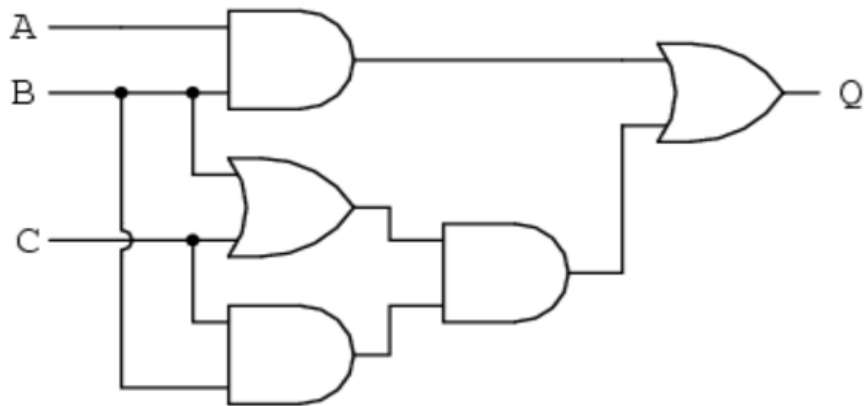
# Boolean Algebra Exercise 1

- Find the direct Boolean expression for the following circuit
- Simplify the Boolean expression using Boolean algebra
- Draw the new circuit for the simplified Boolean expression


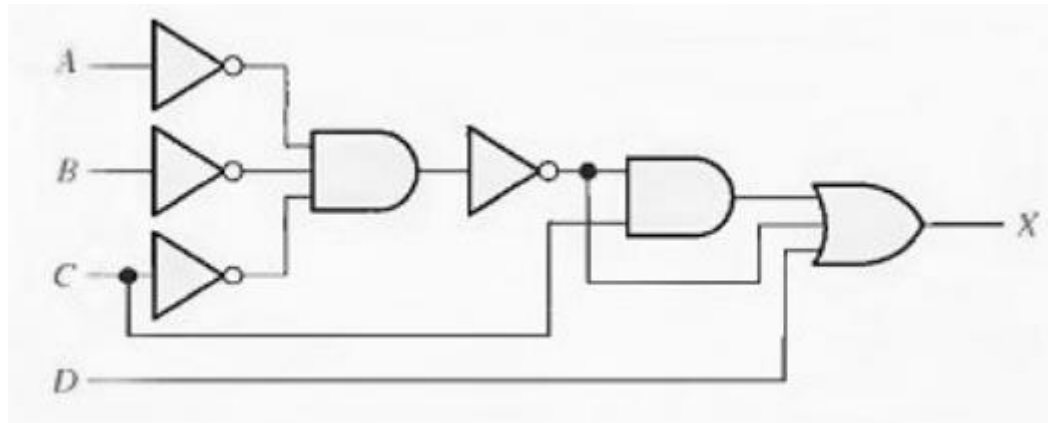
## Boolean Algebra Exercise 2

- Simplify the combinational logic circuit shown below to a minimum form





# Boolean Algebra Exercise 3


---

- Simplify the following Boolean expression

$$AB + \overline{A}BCD + \overline{C}DEF$$
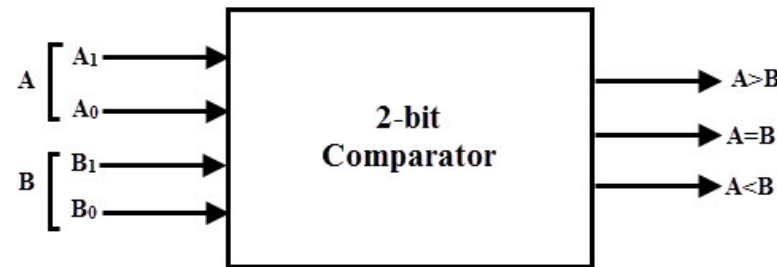
## 2-bit Comparator

- Here we'll be designing circuits to compare 2-bit binary numbers.
- Suppose we have two 2-bit numbers A & B at the inputs, and three outputs as  $A > B$ ,  $A = B$ ,  $A < B$
- Only one of the three outputs would be true accordingly if A is greater than or equal to or less than B.
- We'll practice the circuit design for  $f(A = B)$ , try to work on  $f(A > B)$  and  $f(A < B)$  by yourself



# Solution: 2-bit Comparator Truth Table

$A(A_1A_0)$	$B(B_1B_0)$	$f(A > B)$	$f(A == B)$	$f(A < B)$

# Solution: Logic Function for $f(A==B)$

---




# Solution: Circuit for $f(A==B)$

---


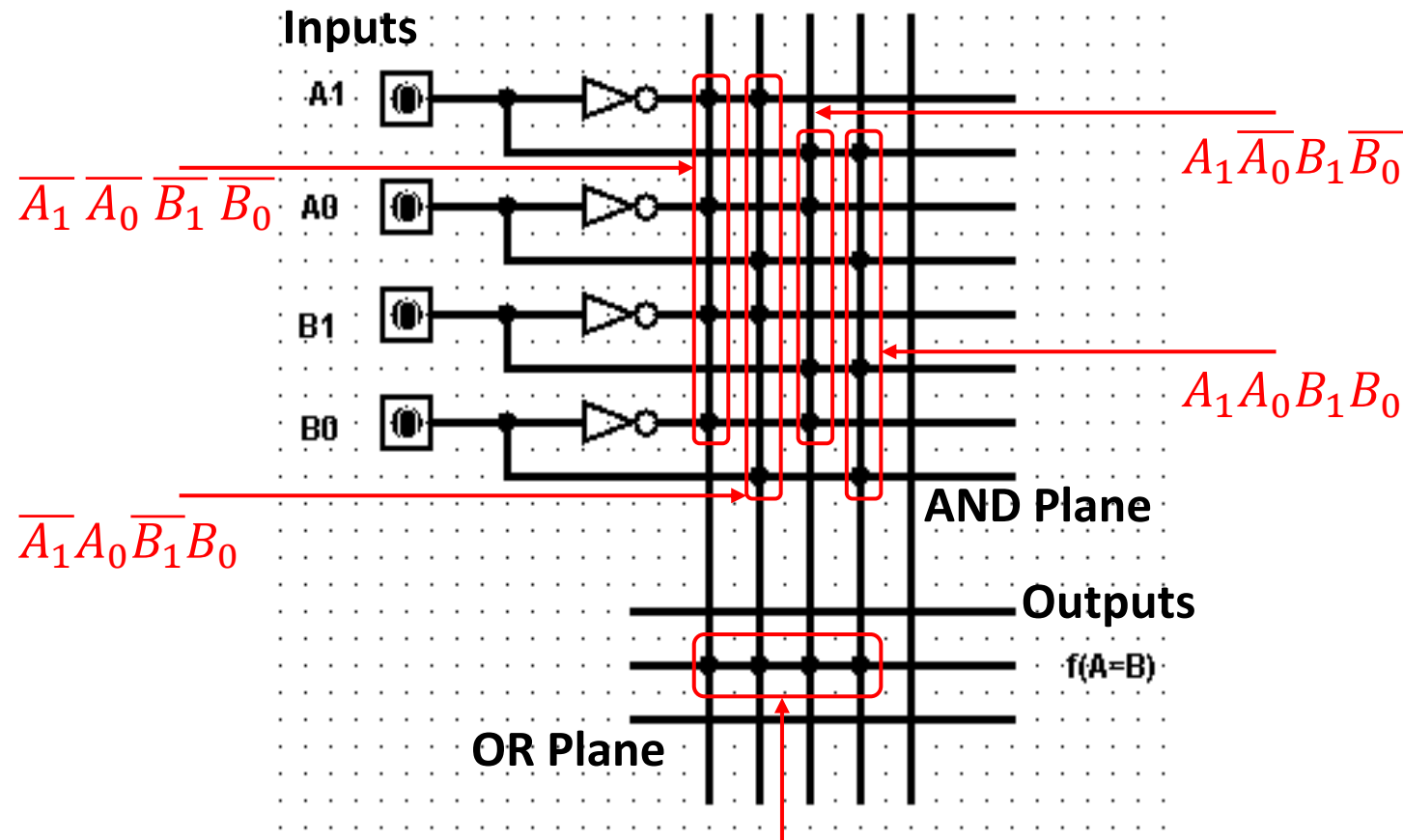
# Solution: PLA Implementation


- The same circuit can be equivalently represented by a **programmable logic array (PLA)** circuit.



$$f(A == B) = \overline{A_1} \overline{A_0} \overline{B_1} \overline{B_0} + \overline{A_1} A_0 \overline{B_1} B_0 + A_1 \overline{A_0} B_1 \overline{B_0} + A_1 A_0 B_1 B_0$$
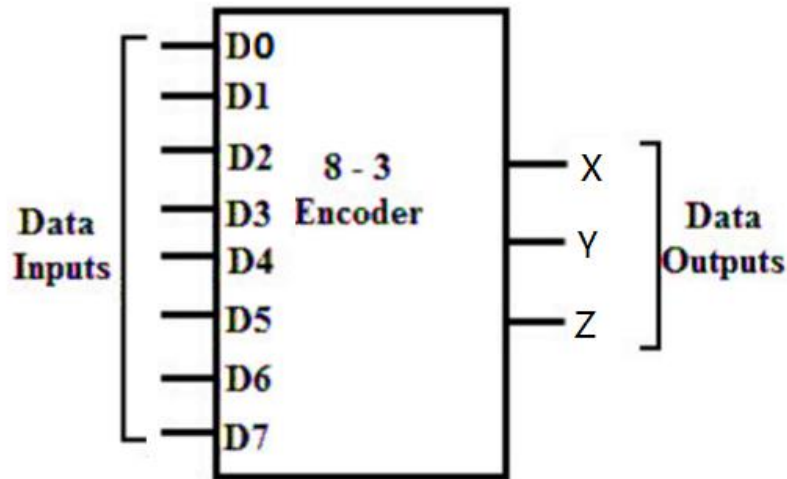
# 8-to-3 Encoder

- An encoder ( $2^N$ -to- $N$  encoder) is a logical block with an  $2^N$ -bit input and  $N$  1-bit outputs, which performs the inverse function of a decoder.
- Example (8-to-3 encoder)
  - 8 inputs ( $D_0, D_1, \dots, D_7$ ) and 3 outputs ( $X, Y, Z$ )



# 8-to-3 Encoder Truth Table

---

$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	X	Y	Z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1




# Solution: Logic Function and Circuit

---


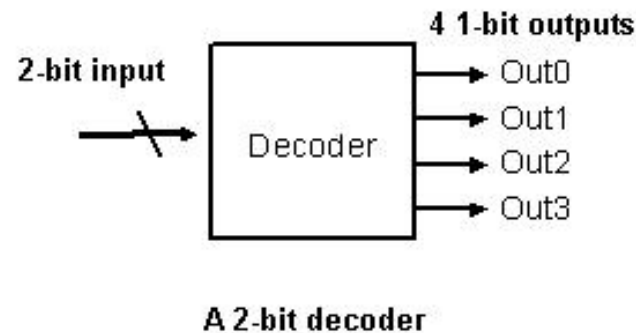
## Extra Exercise: Decoder

- A decoder takes a single  $N$ -bit input and outputs  $2^N$  1-bit signals. The 1-bit output corresponds to the  $N$ -bit input bit pattern is true while all other outputs are false.
- The following figure shows a block diagram for a 2-to-4 decoder.




# Questions

---

- Why a 2-bit input can generate 4 outputs in the decoder?
- If the input bits are 11, what will happen to the outputs of the decoder?
- Is it possible to have more than one outputs asserted?
- Name two potential uses of the decoder.
- Implement the decoder using Logisim.
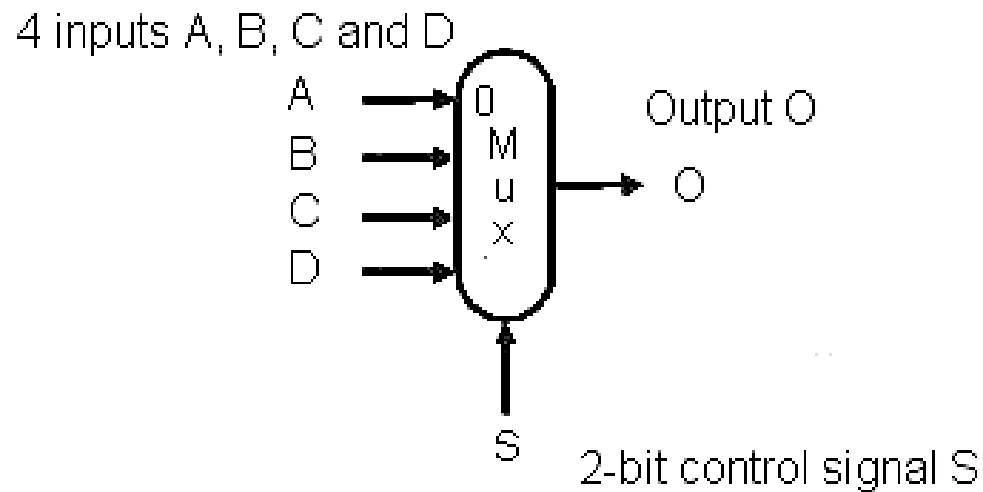
## Extra Exercise: Multiplexor

- A multiplexor is a device that given the control signal, selects one of the inputs to be forwarded to the output. The following figure shows a 4-input multiplexor.
- 4-to-1 multiplexor



# Questions

---

- If the inputs A/B are 32-bit in width, what is the data width of the Output O?
- What is the maximum number of inputs if the control signal is 10-bit in width?
- What is the bit-width of the control signal for the multiplexor if there are 9 inputs?

