

TUTORIAL 1 COMBINATIONAL LOGIC CIRCUIT

Overview

- **We will review the following concept in this tutorial:**
- **Combinational logic circuit**
 - No memory, output(s) solely determined by input(s)
- **Truth table and logic function**
- **Two-level logic and PLA**
- **Simplification with Boolean Algebra and K-map**
- **Circuit design**

- **Work with two practical examples**
 - Bit comparator
 - Encoder

Digital Logic Circuit

■ Two types of digital logic circuits inside a computer:

□ **Combinational logic circuits**

- Logic circuits that do not have memory
- The output depends only on the current inputs and the circuit
- They can be specified fully with a truth table or a logic equation

□ **Sequential logic circuits**

- Logic circuits that have memory
- The output depends on both the current inputs and the value stored in memory (called **state**)



Circuit Design Process

- **A simple logic design process involves**
 - Problem specification
 - Truth table derivation
 - Derivation of logical expression
 - Simplification of logical expression
 - Implementation

Review of Boolean Algebra


- **Boolean algebra consists of**
 - Boolean variables (with values equal to either '0' or '1')
 - Binary operators: AND (\cdot), OR ($+$), NOT ($'$)
- **Any logic function can be expressed as a two-level logic expression, either as**
 - Sum-of-Products (SoP) representation, or
 - Product-of-Sums (PoS) representation
- **The AND, OR, and NOT operations form a functionally complete set (namely, **universal gates**), as they can specify any logic function.**

Basic Laws of Boolean Algebra

Name	AND Form	OR Form
Identity Law	$1A = A$	$0 + A = A$
Null Law	$0A = 0$	$1 + A = 1$
Idempotent Law	$AA = A$	$A + A = A$
Inverse Law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative Law	$AB = BA$	$A + B = B + A$
Associative Law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive Law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption Law	$A(A + B) = A$	$A + AB = A$
De Morgan's Law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}\bar{B}$


Boolean Algebra Exercise 1

 - Find the direct Boolean expression for the following circuit
- Simplify the Boolean expression using Boolean algebra
- Draw the new circuit for the simplified Boolean expression




Boolean Algebra Exercise 1

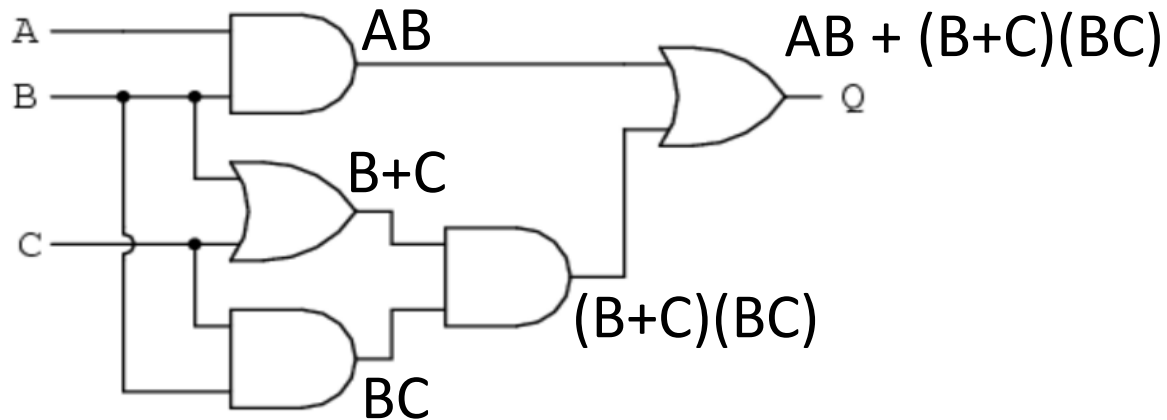- Find the direct Boolean expression for the following circuit
- Simplify the Boolean expression using Boolean algebra
- Draw the new circuit for the simplified Boolean expression



 
$$\begin{aligned} Q &= AB + (B+C)(BC) \\ &= AB + BBC + BCC \\ &= AB + BC + BC \\ &= AB + BC \\ &= B(A+C) \end{aligned}$$




Boolean Algebra Exercise 2

 - Simplify the combinational logic circuit shown below to a minimum form



Boolean Algebra Exercise 2

 - Simplify the combinational logic circuit shown below to a minimum form




$$M = \overline{\overline{A}\overline{B}\overline{C}} = A + B + C$$

Using De Morgan's Law (Bubble Pushing)

$$\begin{aligned} N &= CM = C(A + B + C) \\ &= AC + BC + CC \\ &= AC + BC + C \\ &= C(A + B + 1) \\ &= C(1) = C \end{aligned}$$

$$\begin{aligned} X &= D + M + N \\ &= D + (A + B + C) + C \\ &= A + B + C + D \end{aligned}$$

De Morgan's Law (Bubble Pushing)

 

- Not Gates before and after AND/OR gates can be represented just as the “Bubble”.
- “Convert” the gate between AND/OR, as well as invert the “Bubbles” at all the inputs and the output.
- $\overline{A + B} = \overline{A}\overline{B}$
- $\overline{AB} = \overline{A} + \overline{B}$
- $\overline{\overline{A}\overline{B}\overline{C}} = A + B + C$

Boolean Algebra Exercise 3

- Simplify the following Boolean expression

$$AB + \overline{A}BCD + \overline{C}DEF$$

Boolean Algebra Exercise 3

- Simplify the following Boolean expression

$$\begin{aligned} & AB + \overline{A}BCD + \overline{C}DEF \\ &= (AB(1 + CD)) + \overline{A}BCD + \overline{C}DEF \\ &= (AB + ABCD) + \overline{A}BCD + \overline{C}DEF \\ &= AB + (ABCD + \overline{A}BCD) + \overline{C}DEF \\ &= AB + CD(AB + \overline{A}) + \overline{C}DEF \\ &= AB + CD + \overline{C}DEF \\ &= AB + (CD + CDEF) + \overline{C}DEF \\ &= AB + CD + EF(CD + \overline{C}D) \\ &= AB + CD + EF \end{aligned}$$

Boolean Algebra Exercise 3 (Truth Table)

- **Simplification via Boolean Algebra axioms can be tedious.**
 - Especially when the number of inputs increases.
- **Truth Table and K-map can be a faster way to simplify.**
 - See Excel File for full truth table.

Boolean Algebra Exercise 3 (K-map)

Karnaugh Map

<i>X</i>	<i>D,E,F</i>								
		000	001	011	010	110	111	101	100
<i>A,B,C</i> 000	0	0	1	0	0	1	0	0	
001	0	0	1	0	1	1	1	1	
011	0	0	1	0	1	1	1	1	
010	0	0	1	0	0	1	0	0	
110	1	1	1	1	1	1	1	1	
111	1	1	1	1	1	1	1	1	
101	0	0	1	0	1	1	1	1	
100	0	0	1	0	0	1	0	0	

Three groupings:

- Blue: AB
- Green: CD
- Red: EF
- $X = AB + CD + EF$

6-variable K-map adjacency:

- Top and bottom rows.
- Left and right columns.
- Rows and Columns where only 1 input changes, i.e., (011, 111)
- This is why the Green grouping seems disjointed but is actually adjacent. Similar for the Red grouping.




香港科技大學

THE HONG KONG UNIVERSITY OF SCIENCE AND TECHNOLOGY

2-bit Comparator

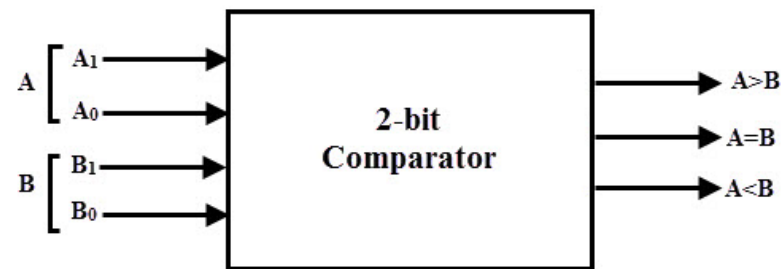- Here we'll be designing circuits to compare 2-bit binary numbers.
- Suppose we have two 2-bit numbers A & B at the inputs, and three outputs as $A > B$, $A = B$, $A < B$
- Only one of the three outputs would be true accordingly if A is greater than or equal to or less than B.
- We'll practice the circuit design for $f(A = B)$, try to work on $f(A > B)$ and $f(A < B)$ by yourself



Solution: 2-bit Comparator Truth Table

A(A ₁ A ₀)	B(B ₁ B ₀)	f (A>B)	f (A==B)	f (A<B)
00	00	0	1	0
00	01	0	0	1
00	10	0	0	1
00	11	0	0	1
01	00	1	0	0
01	01	0	1	0
01	10	0	0	1
01	11	0	0	1
10	00	1	0	0
10	01	1	0	0
10	10	0	1	0
10	11	0	0	1
11	00	1	0	0
11	01	1	0	0
11	10	1	0	0
11	11	0	1	0

Solution: Logic Function for $f(A==B)$

■ Four output rows of $f(A==B)$ that has value of '1':

□ Four corresponding input rows:
(A=00,B=00) , (A=01,B=01) , (A=10,B=10) , (A=11,B=11).

□ The four 1-minterms are:

$$\overline{A_1} \overline{A_0} \overline{B_1} \overline{B_0} , \overline{A_1} A_0 \overline{B_1} B_0 , A_1 \overline{A_0} B_1 \overline{B_0} , A_1 A_0 B_1 B_0$$

■ The output is the OR operation of the four 1-minterms:

$$f(A == B) = \overline{A_1} \overline{A_0} \overline{B_1} \overline{B_0} + \overline{A_1} A_0 \overline{B_1} B_0 + A_1 \overline{A_0} B_1 \overline{B_0} + A_1 A_0 B_1 B_0$$


■ Unfortunately, no further simplification possible.



Solution: Circuit for $f(A==B)$


$$f(A == B)$$
 
$$= \overline{A_1} \overline{A_0} \overline{B_1} \overline{B_0} + \overline{A_1} A_0 \overline{B_1} B_0 + A_1 \overline{A_0} B_1 \overline{B_0} + A_1 A_0 B_1 B_0$$



Solution: PLA Implementation

 
- The same circuit can be equivalently represented by a **programmable logic array (PLA)** circuit.



$$f(A == B) = \overline{A_1} \overline{A_0} \overline{B_1} \overline{B_0} + \overline{A_1} A_0 \overline{B_1} B_0 + A_1 \overline{A_0} B_1 \overline{B_0} + A_1 A_0 B_1 B_0$$

8-to-3 Encoder

 - An encoder (2^N -to-N encoder) is a logical block with an 2^N -bit input and N 1-bit outputs, which performs the inverse function of a decoder.
- Example (8-to-3 encoder)
 - 8 inputs (D_0, D_1, \dots, D_7) and 3 outputs (X, Y, Z)



8-to-3 Encoder Truth Table


D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	X	Y	Z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

Solution: Logic Function and Circuit

□ $X = D_4 + D_5 + D_6 + D_7$


□ $Y = D_2 + D_3 + D_6 + D_7$

□ $Z = D_1 + D_3 + D_5 + D_7$

 

Extra Exercise: Decoder

 - A decoder takes a single N-bit input and outputs 2^N 1-bit signals. The 1-bit output corresponds to the N-bit input bit pattern is true while all other outputs are false.
- The following figure shows a block diagram for a 2-to-4 decoder.



Questions


- Why can a 2-bit input generate 4 outputs in the decoder?
- If the input bits are 11, what will happen to the outputs of the decoder?
- Is it possible to have more than one outputs asserted (=1)?
- Name two potential uses of the decoder.
- Implement the decoder using Logisim.

Questions

- **Why can a 2-bit input generate 4 outputs in the decoder?**
 - $2^2 = 4$.
- **If the input bits are 11, what will happen to the outputs of the decoder?**
 - Out3 = 1, Out2 = 0, Out1 = 0, Out0 = 0.
- **Is it possible to have more than one outputs asserted (=1)?**
 - Logically no for Line Decoders. Can be a feature in special decoders.
- **Name two potential uses of the decoder.**
 - Reduce the number of control lines needed, if only 1-out-of-N devices need to be active at any single timeframe.
 - Convert digital signals to analog signals, e.g., synchronize multiple motors.

Extra Exercise: Multiplexor

 - A multiplexor is a device that given the control signal, selects one of the inputs to be forwarded to the output. The following figure shows a 4-input multiplexor.
- 4-to-1 multiplexor



Questions

- If the inputs A/B are 32-bit in width, what is the data width of the Output O?
- What is the maximum number of inputs if the control signal is 10-bit in width?
- What is the bit-width of the control signal for the multiplexor if there are 9 inputs?

Questions

- If the inputs A/B/C/D are 32-bit in width, what is the data width of the Output O?
 - 32-bit.
- What is the maximum number of inputs if the control signal is 10-bit in width?
 - $2^{10} = 1024$.
- What is the bit-width of the control signal for the multiplexor if there are 9 inputs?
 - 4 bits. $2^4 = 16$, while $2^3 = 8$ is insufficient.